

**Fourth Semester B.E. Degree Examination, June/July 2014**  
**Power Electronics**

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions, selecting atleast TWO questions from each part.**

**PART – A**

- 1 a. Mention and explain the different types of power electronic converter systems and also specify the form of input and output with wave forms. (12 Marks)  
b. With neat sketch explain the operation of H.V.D.C power transmission systems. (08 Marks)
- 2 a. With necessary waveforms explain the switching characteristics of an I.G.B.T. (10 Marks)  
b. In the bipolar transistor circuit shown in Fig.Q.2(b),  $\beta$  varies between 10 to 60. The load resistance  $R_C = 5\Omega$ ,  $V_{CC} = 100V$ ,  $U_{BB} = 8V$ , if  $V_{CE(sat)} = 2.5V$  and  $V_{BE(sat)} = 1.75V$ , calculate:  
i) The value of  $R_B$  that results in saturation with an overdrive factor of 20; ii) The forced  $\beta$  value; iii) Power loss in the transistor. (10 Marks)

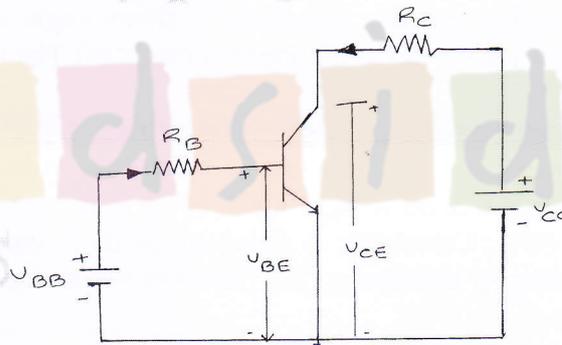


Fig.Q.2(b)

- 3 a. With the help of two transistor model derive an expression for the anode current of a thyristor. (08 Marks)  
b. For the circuit shown in Fig.Q.3(b) if the latching current is 4mA, calculate the minimum width of gate pulse required to properly turn on the SCR. (04 Marks)

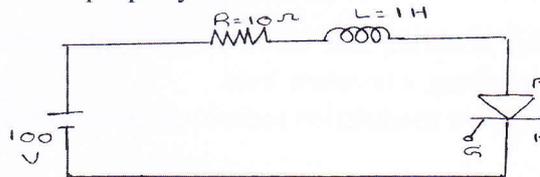


Fig.Q.3(b)

- c. With circuit diagram and wave forms explain the working of U.J.T. triggering technique of SCR. (08 Marks)
- 4 a. With circuit diagram and wave forms explain the resonant pulse commutation. (12 Marks)

- b. Circuit of Fig.Q.4(b) employing class C commutation has  $V_S = 200V$ ,  $R_1 = 10\Omega$  and  $R_2 = 100\Omega$ . Calculate: i) Peak value of current through thyristor  $T_1$ ; ii) The value of capacitor  $C$  if each thyristor has turn off time of  $40 \mu$  sec. Consider factor of safety as 2; iii) Sketch the thyristors voltage wave forms for one complete cycle. (08 Marks)

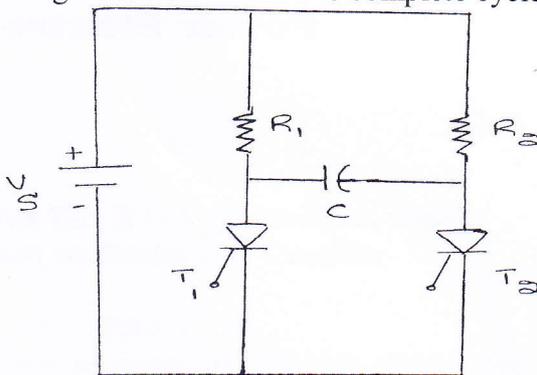


Fig.Q.4(b)

## PART - B

- 5 a. With circuit diagram and wave forms explain the operation of a three phase full wave controlled rectifier with resistive load. And also derive the equation for average value of output voltage. (12 Marks)
- b. A single phase half wave controlled rectifier supplies a purely resistive load of  $10\Omega$ , from a  $230V$ ,  $50Hz$  supply. If the average output voltage is 75% of the maximum possible value of the d.c. output voltage. Calculate: i) Delay angle of thyristors; ii) R.M.S. value of output voltage; iii) RMS value of output current; iv) The input power factor. (08 Marks)
- 6 a. With circuit diagram and quadrant operation, explain four quadrant choppers. (10 Marks)
- b. In the circuit shown in Fig.Q.6(b) the supply voltage is  $240V$ . The voltage drop across the switch when it is on is  $V_S = 1.5V$ . If the load resistance is  $R = 15\Omega$ ,  $f = 1.2$  KHZ and duty cycle is 60%. Calculate: i) The average d.c. output voltage; ii) the r.m.s. output voltage; iii) The chopper efficiency; iv) The input resistance of the chopper. (10 Marks)

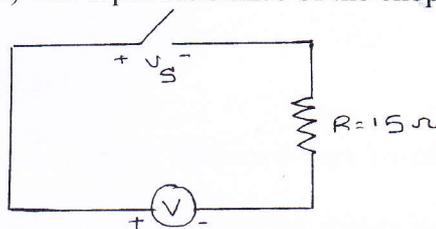


Fig.Q.6(b)

- 7 a. With circuit diagram and wave forms explain the operation of a single phase full bridge inverter supplying a resistive load. (10 Marks)
- b. Explain any two modulation techniques available for voltage control a single phase inverter. (10 Marks)
- 8 a. With circuit diagram and wave forms explain the operation of a bidirectional controller with RL load. (10 Marks)
- b. A single phase full wave a.c. voltage controller has an input voltage of  $230V$  and a load resistance of  $10\Omega$ . The firing angle is  $90^\circ$ . Calculate: i) RMS output voltage; ii) RMS output current; iii) Output power; iv) The input power factor; v) Average thyristor current. (10 Marks)

\*\*\*\*\*